

## Logic Design I

CSci 2021: Machine Architecture and Organization  
Lecture #36, April 24th, 2015

Your instructor: Stephen McCamant

1

## Brief History of Computing Machines

- **1800s: purely mechanical**
  - General-purpose computer designed, but not fully built
- **1940s: first general-purpose computers**
  - Electromechanical relays
  - Vacuum tubes
  - Idea: electrically-controlled electric switch
- **1947: transistor**
  - "Solid state": no moving parts or gases
  - Based on semiconducting materials like silicon
  - Can be used as a switch or an amplifier
  - Takes a lot to make a computer...

2


## Integrated Circuits

- **Key technology for inexpensive computing**
  - Printing transistors (and other devices) on a silicon wafer
- **Low incremental production cost**
  - But the design and the factory are expensive
- **Long history of increasing density**
  - First ICs had <100 devices per chip
  - Moore's law: exponential increase in # of transistors per device
    - Doubling every 12-24 months
  - Modern CPU: tens of billions of transistors

3
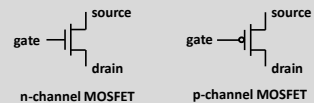
## MOSFETs


- **Modern kind of transistor used in ICs**
  - Metal-oxide-semiconductor field-effect transistor



- **Voltage at the gate determines whether current can flow between source and drain**
  - n-channel type: high voltage allows current to flow
  - p-channel type: low voltage allows current to flow


4

## Transistors To Gates: CMOS Inverter

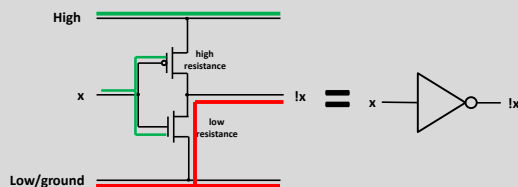


5

## Transistors To Gates: CMOS Inverter

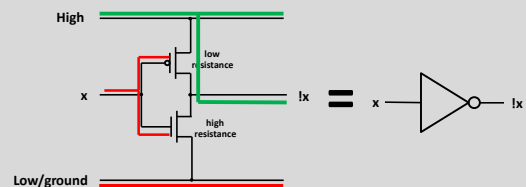

6

## CMOS NAND Gate

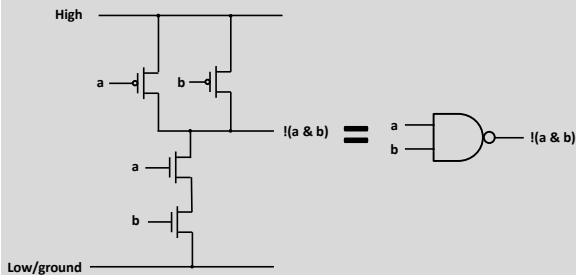

7


## Logistics Note: (No) Readings

- Most of this material is not in the textbook
- We've posted links to free online resources
  - On the "Useful" page of the main course site
- Will post specific suggestions for readings in "All About Circuits, Volume 4"
- But readings cover much material you don't need to know
  - Lecture notes are guide to assignment and test coverage


8
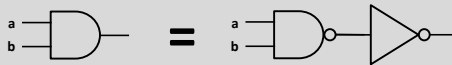
## Getting to AND and OR

- This is enough to build any circuit
- AND = NAND + NOT



- OR = NOT + NOT + NAND

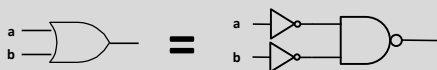

9

## One-input One-output Gates

- What are the possibilities?  $2^2 = 4$  choices

x	f(x)
0	0
1	0

Always false.  
Boring.

x	f(x)
0	1
1	1

Always true.  
Boring.

x	f(x)
0	0
1	1

Just like a wire.  
Boring.

x	f(x)
0	1
1	0

Inverter.  
Least boring.

10

## Two-input One-output Gates (1)

- $2^4 = 16$  possibilities. First some boring ones:

	0	1
0	0	0
1	0	0

Always 0

	0	1
0	0	0
1	1	1

x

	0	1
0	0	1
1	0	0

!x

	0	1
0	0	1
1	1	1

Always 1

	0	1
0	0	0
1	0	1

y

	0	1
0	0	1
1	1	0

!y

11

## Two-input One-output Gates (2)

- Symmetric cases:

	0	1
0	0	0
1	0	1

AND

	0	1
0	0	0
1	1	1

OR

	0	1
0	0	0
1	1	0

XOR, !=

	0	1
0	0	1
1	1	0

NAND

	0	1
0	0	1
1	0	0

NOR

	0	1
0	0	1
1	1	0

XNOR, ==

12

## Two-input One-output Gates (3)

### Asymmetric cases:

x\y	0	1
0	1	1
1	0	1

$x \rightarrow y, !x | y$

x\y	0	1
0	0	0
1	1	0

$!(x \rightarrow y), x \& !y$

x\y	0	1
0	1	0
1	1	1

$y \rightarrow x, !y | x$

x\y	0	1
0	0	1
1	0	0

$!(y \rightarrow x), y \& !x$

13

## Boolean Algebra

### Boolean algebra

- Boolean functions (gates) have a nice algebraic structure
- But it's different from the rules for arithmetic
- Same algebraic structure applies to sets, Boolean functions

### Boolean algebra and other notations

- $0 = \perp$
- $1 = \top$
- $\& = \wedge$ , also sometimes  $\cdot$
- $| = \vee$
- $\wedge = \oplus$
- $! = \neg, \sim$ , or a line above, or ' suffix
- "+" is ambiguous: electrical engineers often use it for OR, but mathematicians use it for XOR

14

## Boolean Identities (1)

- $(x | x) = x$
- $(x | 1) = 1$
- $(x | 0) = x$
- $|$  is associative
- $|$  is commutative
- $(x | !x) = 1$
- $a \& (b | c) = (a \& b) | (a \& c)$
- $!(a \& b) = (!a | !b)$
- $(x \& x) = x$
- $(x \& 0) = 0$
- $(x \& 1) = x$
- $\&$  is associative
- $\&$  is commutative
- $(x \& !x) = 0$
- $a | (b \& c) = (a | b) \& (a | c)$
- $!(a | b) = !a \& !b$
- Duality principle:** given a formula using  $\&$ ,  $|$ , and  $!$ , it's also true if you swap  $\&$  with  $|$  and 0 with 1

15

## Boolean Identities (2)

- $!!x = x$
- $\wedge$  is commutative
- $\wedge$  is associative
- $(x \wedge x) = 0$
- $(x \wedge 0) = x$
- $(x \wedge 1) = !x$
- $!(a \wedge b) = (!a \wedge !b) = (a \wedge !b)$

$\wedge$  forms an Abelian group with identity 0; the inverse of  $x$  is  $x$

16

## Universal Sets of Gates

- A set of gates is *universal* if any Boolean function can be constructed from just gates in the set
  - {AND, OR, NOT} is universal; proof coming later
  - {AND, NOT} and {OR, NOT} are universal
    - Use DeMorgan's laws
  - {NAND, NOT} is universal
    - Make AND from NAND and NOT
  - {NAND} is universal
    - $!x = !(x \& x)$
  - {NOR, NOT} and {NOR} are universal
  - {AND, OR} is not universal
  - {XOR, NOT} is not universal

17

## Truth Tables

- Combinational circuit = Boolean function**
  - Combinational: no cycles or memory
  - Outputs are determined just by inputs
- Finite size**
  - A Boolean function has a finite representation
  - If  $i$  input bits,  $2^i$  possible input combinations
  - Can study by just writing the output for all possible inputs
- Truth table**
  - Standard way to write a function
  - $2^i$  rows, input combinations in increasing order
  - One column per intermediate or output

18

## Truth Table Example

a	b	c	(a & b)	(a & b)   c
0	0	0	0	0
0	0	1	0	1
0	1	0	0	0
0	1	1	0	1
1	0	0	0	0
1	0	1	0	1
1	1	0	1	1
1	1	1	1	1

19

## Equivalences with a Truth Table

- **Check whether two Boolean formulas are equal**
  - Write truth table covering both
  - Check two columns have all the same entries
- **Advantages**
  - Straightforward
  - No algebraic insight needed
- **Disadvantages**
  - Effort exponential in number of input bits

20

## Equivalence Example

a	b	c	(b & c)	a   (b & c)	(a   b)	(a   c)	(a   b) & (a   c)
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	1	0	0
0	1	1	1	1	1	1	1
1	0	0	0	1	1	1	1
1	0	1	0	1	1	1	1
1	1	0	0	1	1	1	1
1	1	1	1	1	1	1	1

21

## Combinational Logic Design

- **Given: description of circuit behavior**
  - Word problem, or truth table
- **Goal: efficient circuit implementation**
  - Usually most important: fewest gates and wires
  - Secondly: reduce number of levels (propagation delay)
- **Kinds of techniques**
  - Up to 6 inputs: pencil and paper approaches
  - Large but structured: split into repeated pieces
  - Large and unstructured: computer algorithm

22